



《计算机系统结构》课程直播

2020.4.7

请将ZOOM名称改为“姓名”；

听不到声音请及时调试声音设备；签到将在课结束后继续

讲课内容

1

单周期处理器的设计

课堂讨论

- 解释为什么汇编程序在对下列汇编源程序中的beq指令进行汇编时会遇到问题，应该如何修改该程序段？

```
here:  beq $s0, $s2, there
```

```
.....
```

```
there:  addi $s1, $s0, 4
```

处理器设计



□ 能实现几条简单指令的处理器

算术逻辑运算指令: **add, sub, ori**

访问存储器: **lw, sw**

控制流指令: **beq, j**

MIPS指令的子集

■ 加法与减法

- `add rd, rs, rt`
- `sub rd, rs, rt`

■ OR 立即数:

- `ori rt, rs, imm16`

■ 读内存 和 写内存

- `lw rt, rs, imm16`
- `sw rt, rs, imm16`


■ 条件转移:

- `beq rs, rt, imm16`


■ 无条件转移:

- `j target`

R 型:

 

I 型:

 

J 型:



设计处理器的五个步骤






   1. 分析指令系统，得出对数据通路的需求
2. 选择数据通路上合适的组件
3. 连接组件构成数据通路
4. 分析每一条指令的实现，以确定控制信号
5. 集成控制信号，完成控制逻辑


Hardware Elements




- Combinational logic:
 - Output is a function of the present input only: Out



 
- Synchronous sequential logic
 - Edge-triggered: data is sampled at the clock edge



D	CLK	Q
0	Rising	0
1	Rising	1
-	0	Last Q
-	1	Last Q

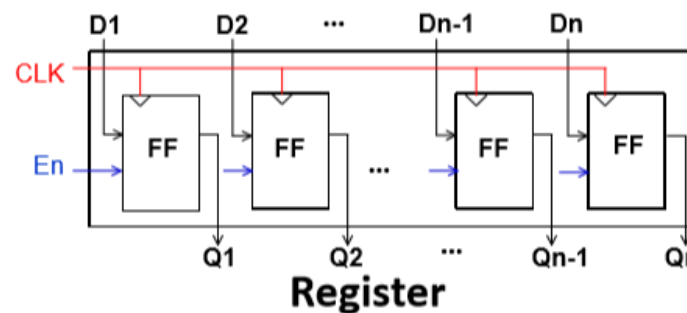



Register Files

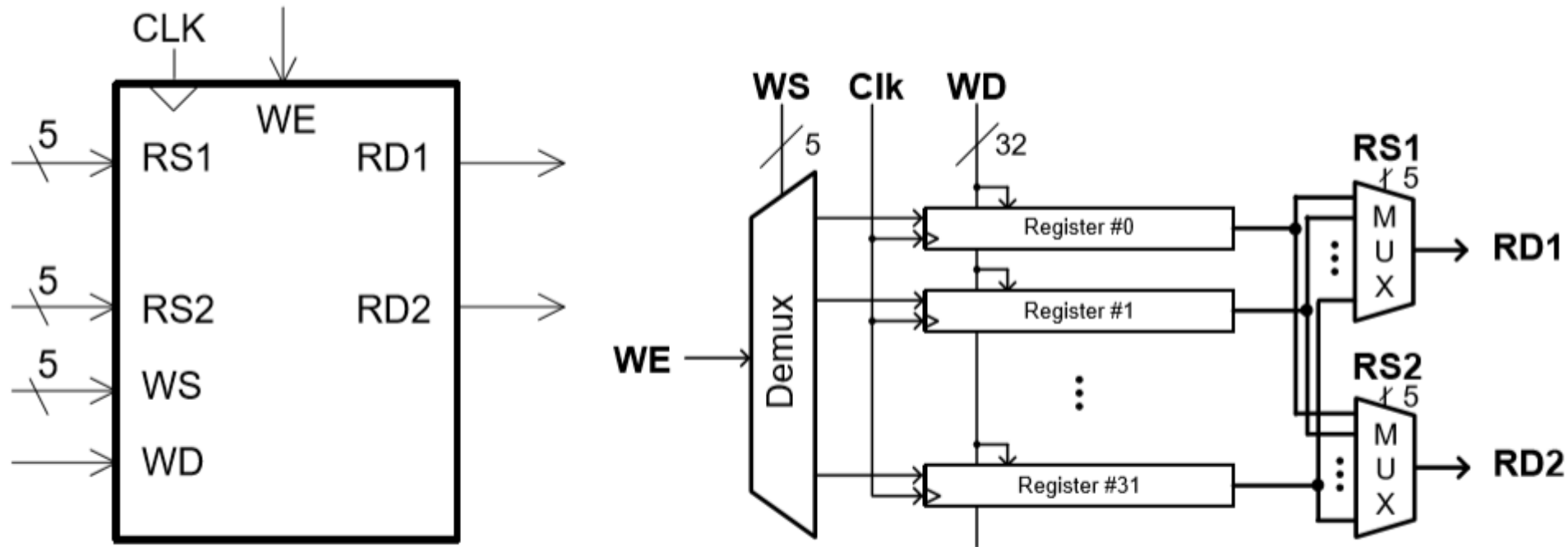


- The processor's general-purpose registers are stored in a structure called a **register file**

A Simple Memory Model

  - a Read can be done any time (i.e. combinational logic)
- a Write is performed at the rising clock edge




Harvard Architecture

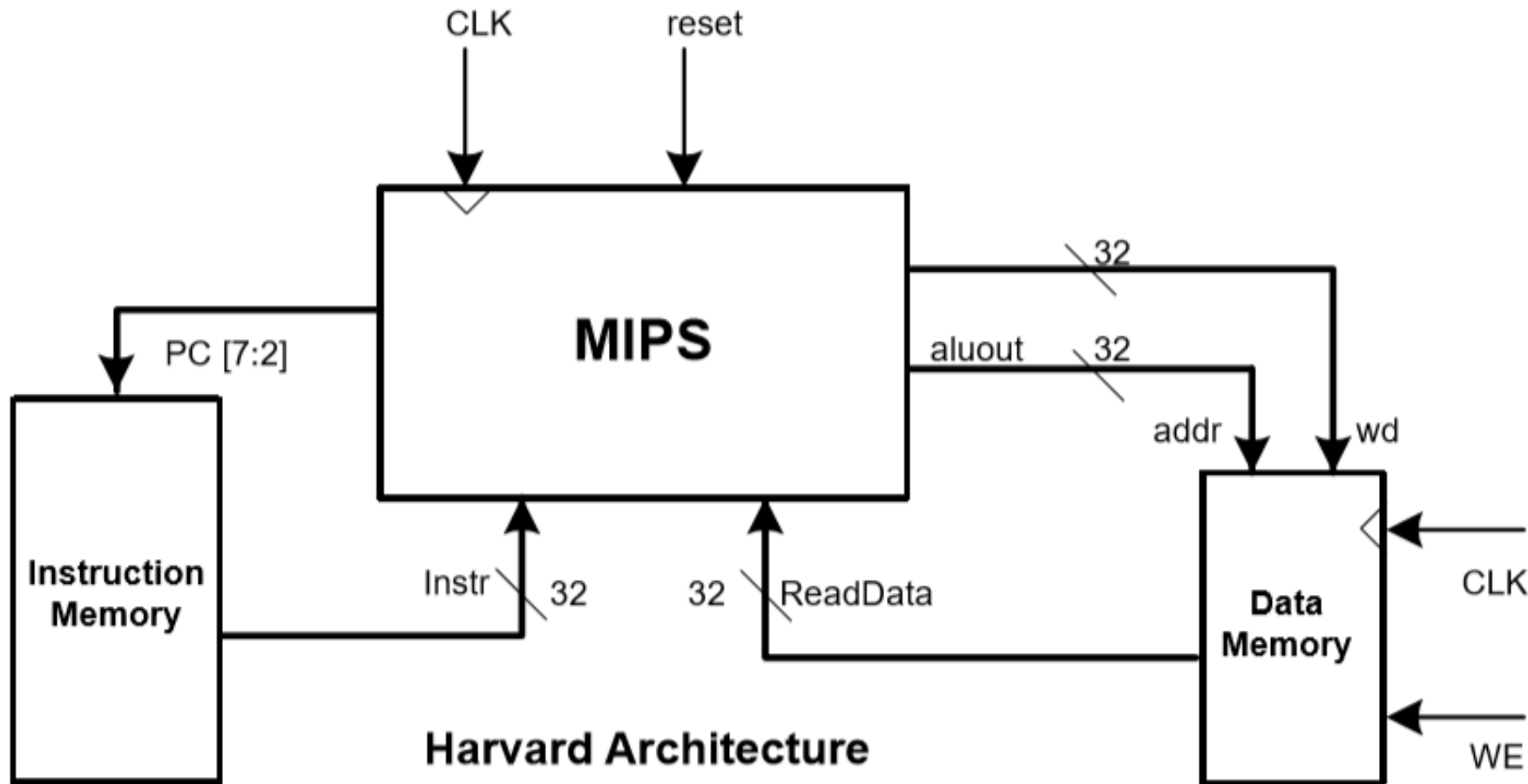


- **Harvard Style:**
Physically separate storage and signal pathways for instructions and data
- **Princeton Style:**
The same pathways (von Neumann Model)

完整的数据通路

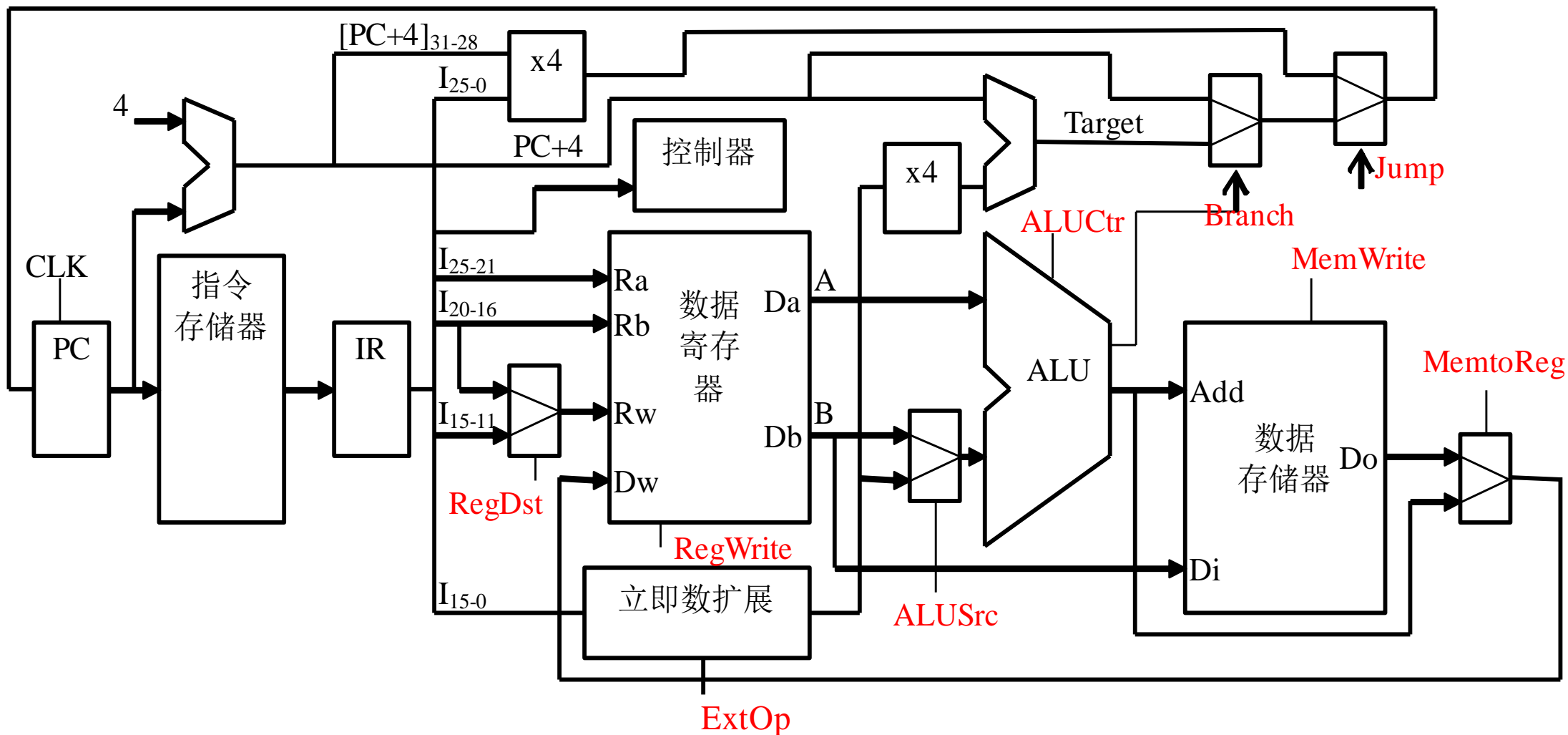

Control Logic

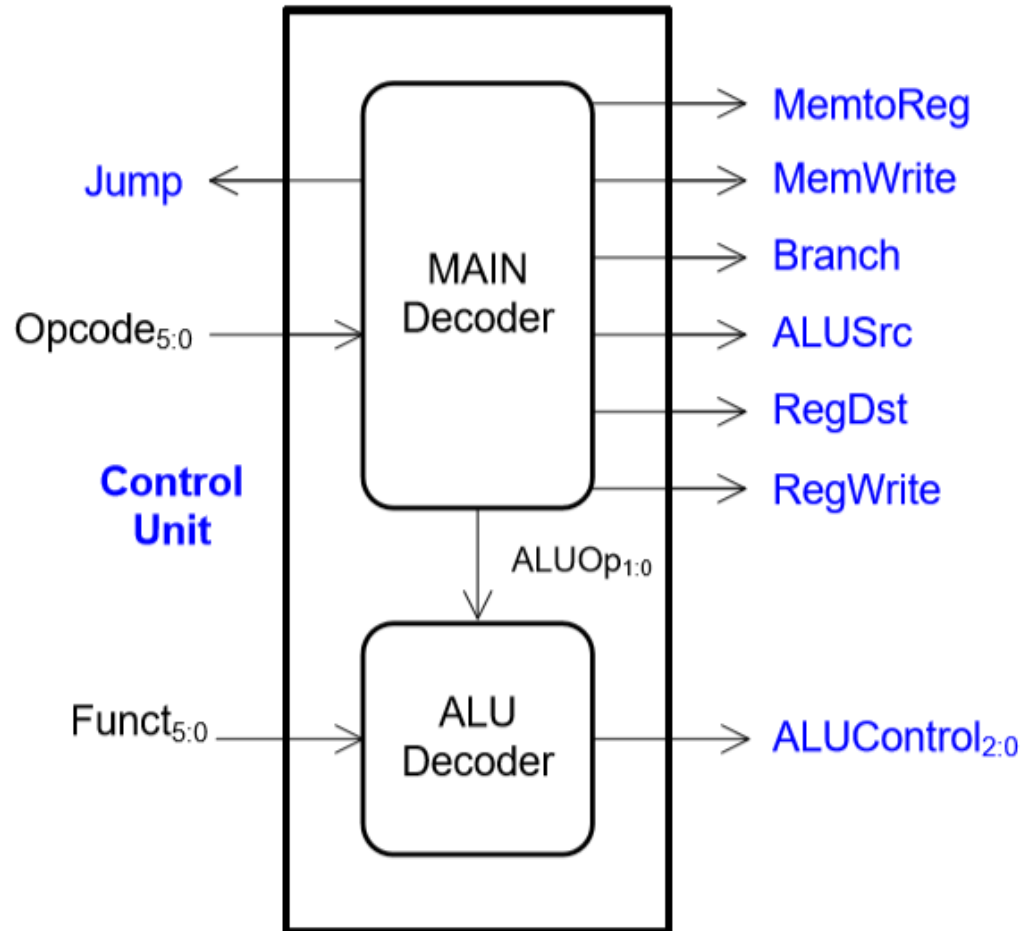

- The setting of the control lines is completely determined by the opcode fields of the instruction
- Focus on the design of the state machines to decode instructions and generate the sequence of control signals


指令 数据通路

ADD $PC \leftarrow PC + 4$

控制信号: **Branch = 0, Jump=0,**

$R[rd] \leftarrow R[rs] + R[rt];$

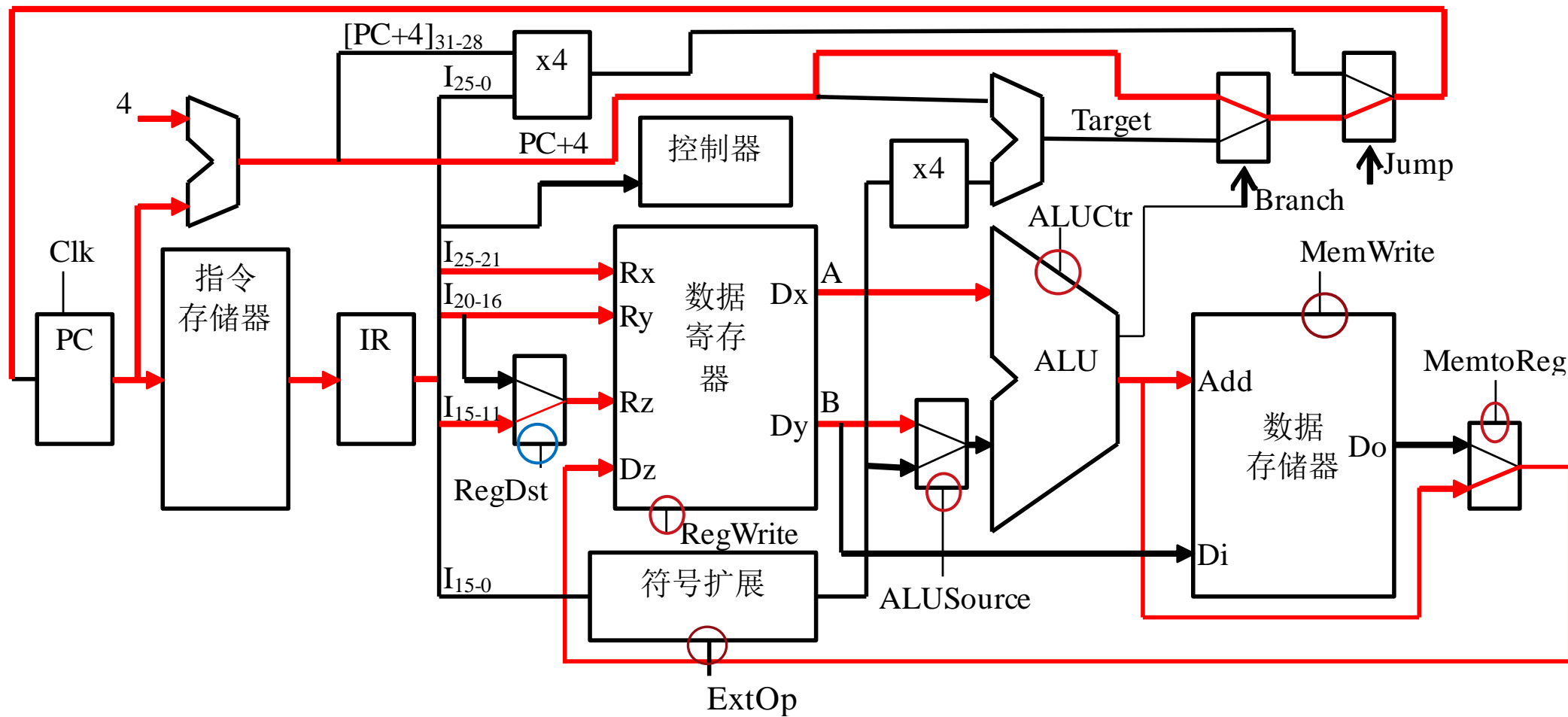ALUsrc = BusB, ALUctr = "add", Extop=x,
Memwrite=0, MemtoReg=ALU, RegDst = rd, RegWr=1




指令 数据通路

Ori $PC \leftarrow PC + 4$

控制信号: $PC_source = 0, Jump=0,$

$R[rt] \leftarrow R[rs] \text{ or } \text{unsign_ext}(\text{Imm16});$

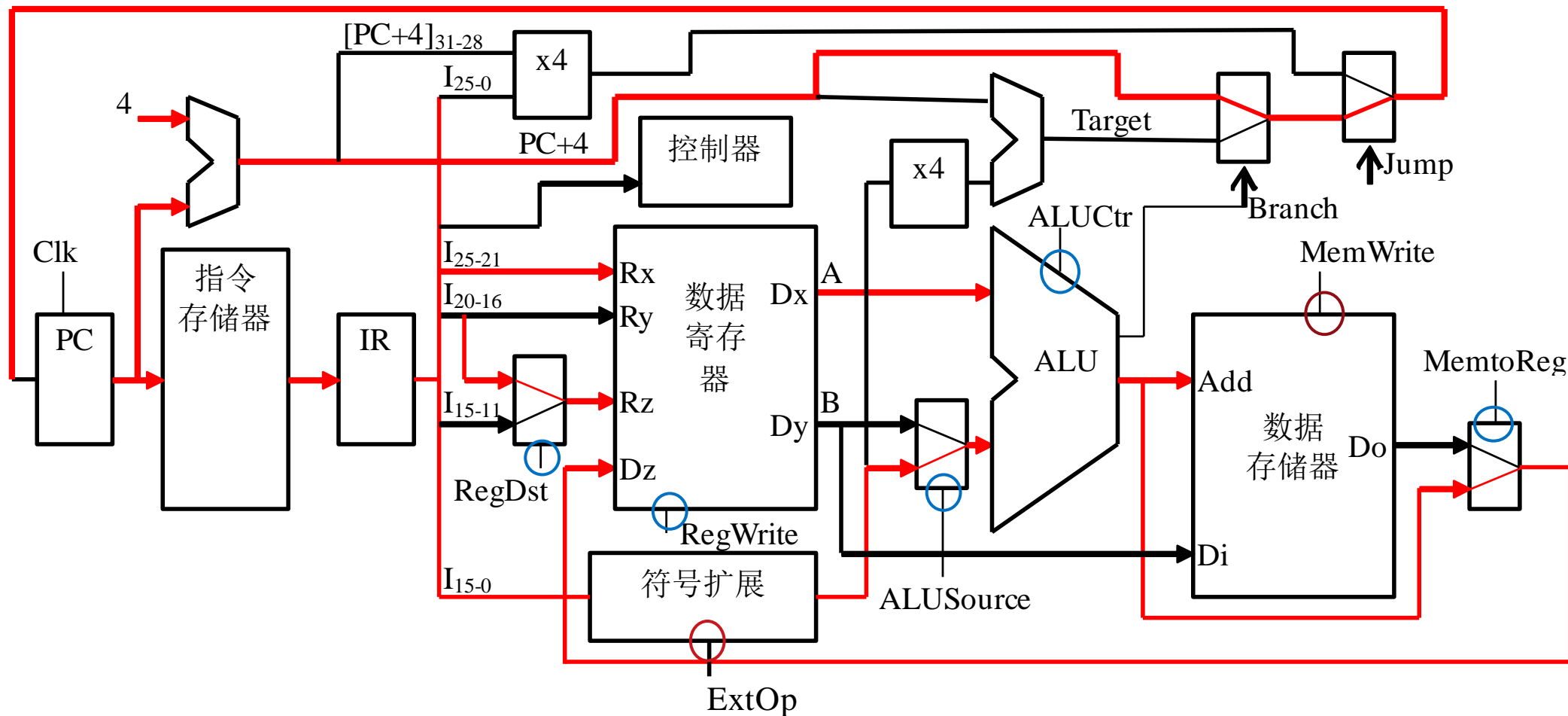$ALUsrc = Im, ALUCtr = \text{"or"}, Extop = \text{"unSn"},$
 $Memwite=0, MemtoReg=ALU, RegDst = rt, RegWr=1$




指令 数据通路

LOAD $PC \leftarrow PC + 4$,

控制信号: **Branch = 0 , Jump=0,**

$R[rt] \leftarrow MEM[R[rs] + \text{sign_ext}(\text{Imm16})];$

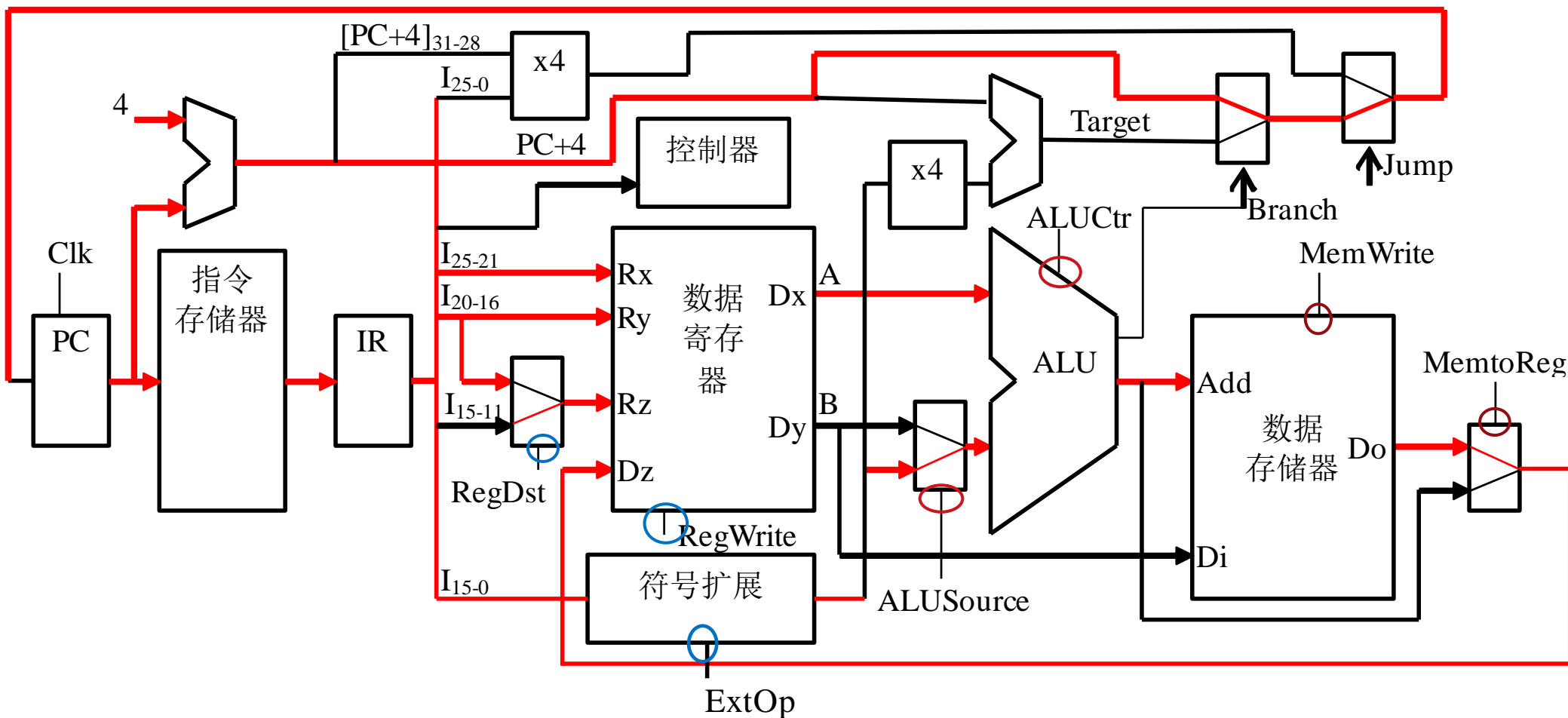**ALUSrc = Im, ALUctr= "add", Extop = "Sn",
Memwrite=0, MemtoReg=Mem, RegDst = rt, RegWr=1**



指令 数据通路


STORE $PC \leftarrow PC + 4$,

控制信号: **Branch = 0 , Jump=0,**

$MEM[R[rs] + \text{sign_ext}(\text{Imm16})] \leftarrow R[rs];$

ALUsrc = Im, ALUctr = "add", Extop = "Sn",

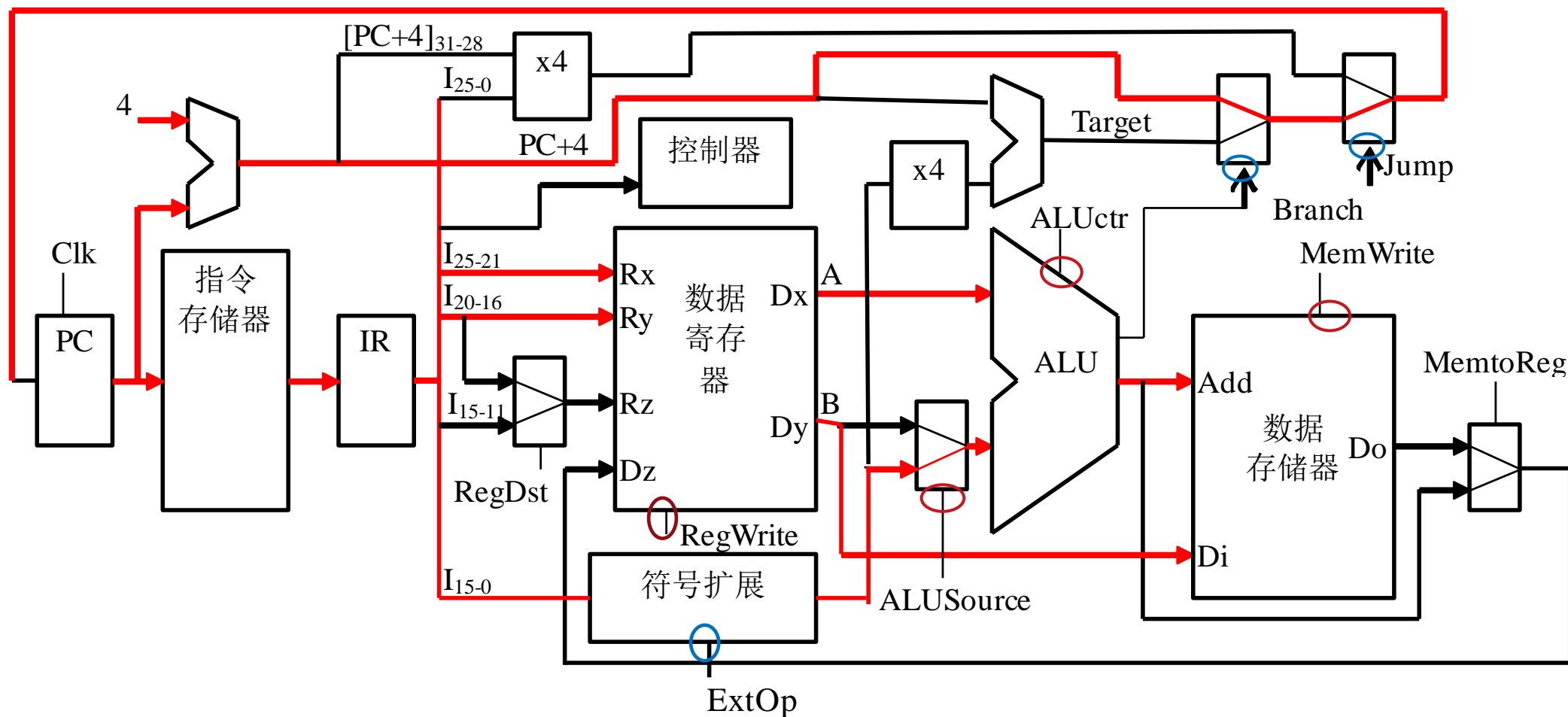
Memwrite=1, MemtoReg=x, RegDst = x, RegWr=0



指令 数据通路

BEQ **if (R[rs] == R[rt]) then PC \leftarrow PC+4 + sign_ext(Imm16)] || 00 else PC \leftarrow PC + 4**

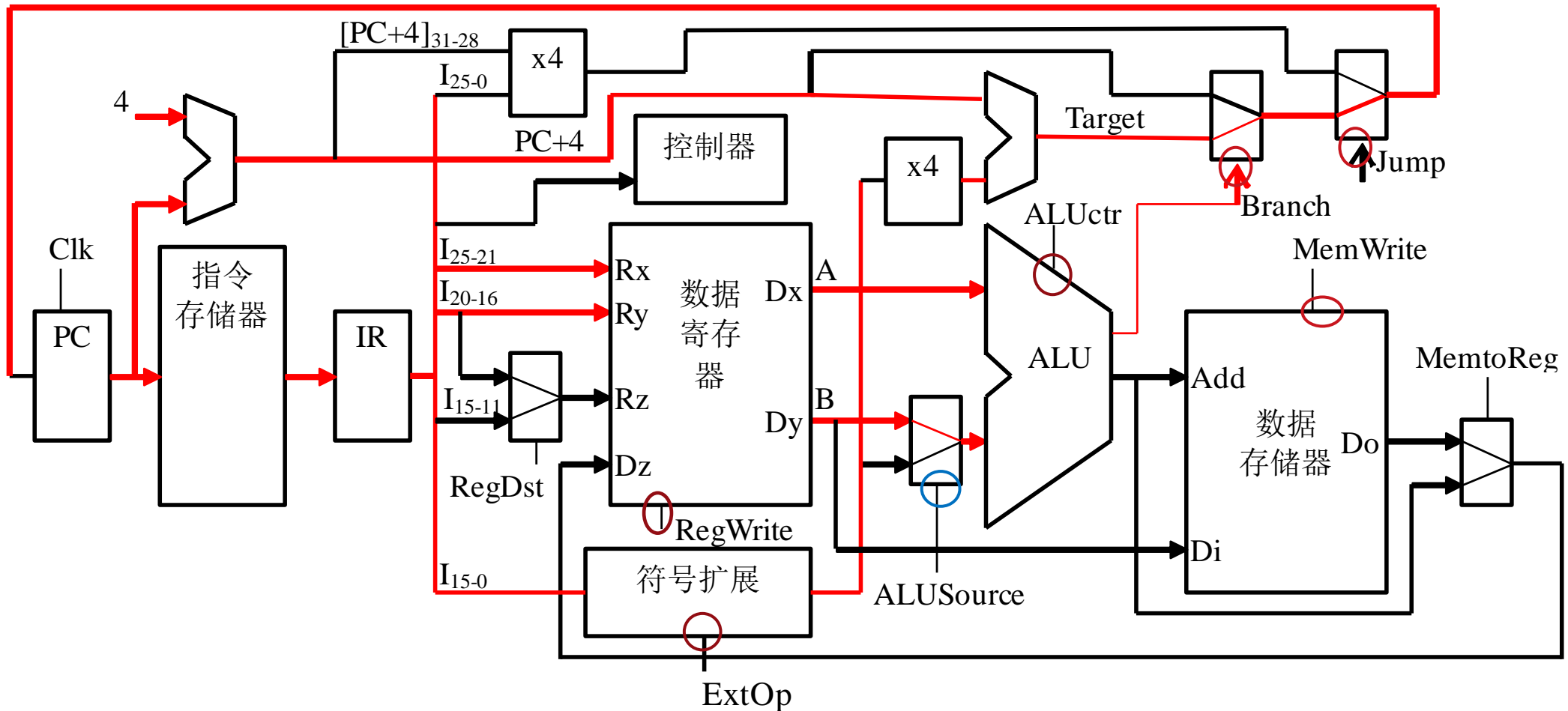
控制信号: **ALUSrc = BusB , ALUctr = "sub" , Extop = "Sn" , Branch = "Br" , Jump=0, Memwrite=0, Regwrite=0, 其余=x**



指令 数据通路

JUMP $PC \leftarrow (PC + 4[31-28], I_{25-0}) \parallel 00$

 控制信号: **Branch=0, Jump=1, Memwrite=0, Regwrite=0, 其余=x**




控制信号总结

指令 数据通路和控制信号:

ADD	$R[rd] \leftarrow R[rs] + R[rt];$	$PC \leftarrow PC + 4$
	Branch = 0 , Jump=0, ALUsrc = BusB , Extop=x, ALUctr = “add”, Memwrite=0, MemtoReg=ALU, RegDst = rd, RegWr=1	
Ori	$R[rd] \leftarrow R[rs] \text{ or } R[rt];$	$PC \leftarrow PC + 4$
	PC_source = 0, Jump=0, Extop = “Sn”, ALUsrc = Im, ALUctr = “or”, Memwite=0, MemtoReg=ALU, RegDst = rt, RegWr=1	
LOAD	$R[rt] \leftarrow \text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})];$	$PC \leftarrow PC + 4$
	Branch = 0 , Jump=0, Extop = “Sn”, ALUsrc = Im, ALUctr= “add”, Memwrite=0, MemtoReg=Mem, RegDst = rt, RegWr=1	
STORE	$\text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})] \leftarrow R[rs];$	$PC \leftarrow PC + 4$
	Branch = 0 , Jump=0, Extop = “Sn”, ALUsrc = Im, ALUctr = “add”, Memwrite=1, MemtoReg=x, RegDst = x, RegWr=0	
BEQ	if ($R[rs] == R[rt]$) then $PC \leftarrow PC + \text{sign_ext}(\text{Imm16}) \parallel 00$ else $PC \leftarrow PC + 4$	
	ALUsrc = BusB , Extop = “Sn”, ALUctr = “sub” , Branch = “Br”, Jump=0, Memwrite=0, Regwrite=0, MemtoReg=x, RegDst = x,	
JUMP	$PC \leftarrow (PC + 4[31-28], I_{25-0}) \parallel 00$	
	Branch=0, Jump=1, Memwrite=0, Regwrite=0, 其余=x	

课堂练习

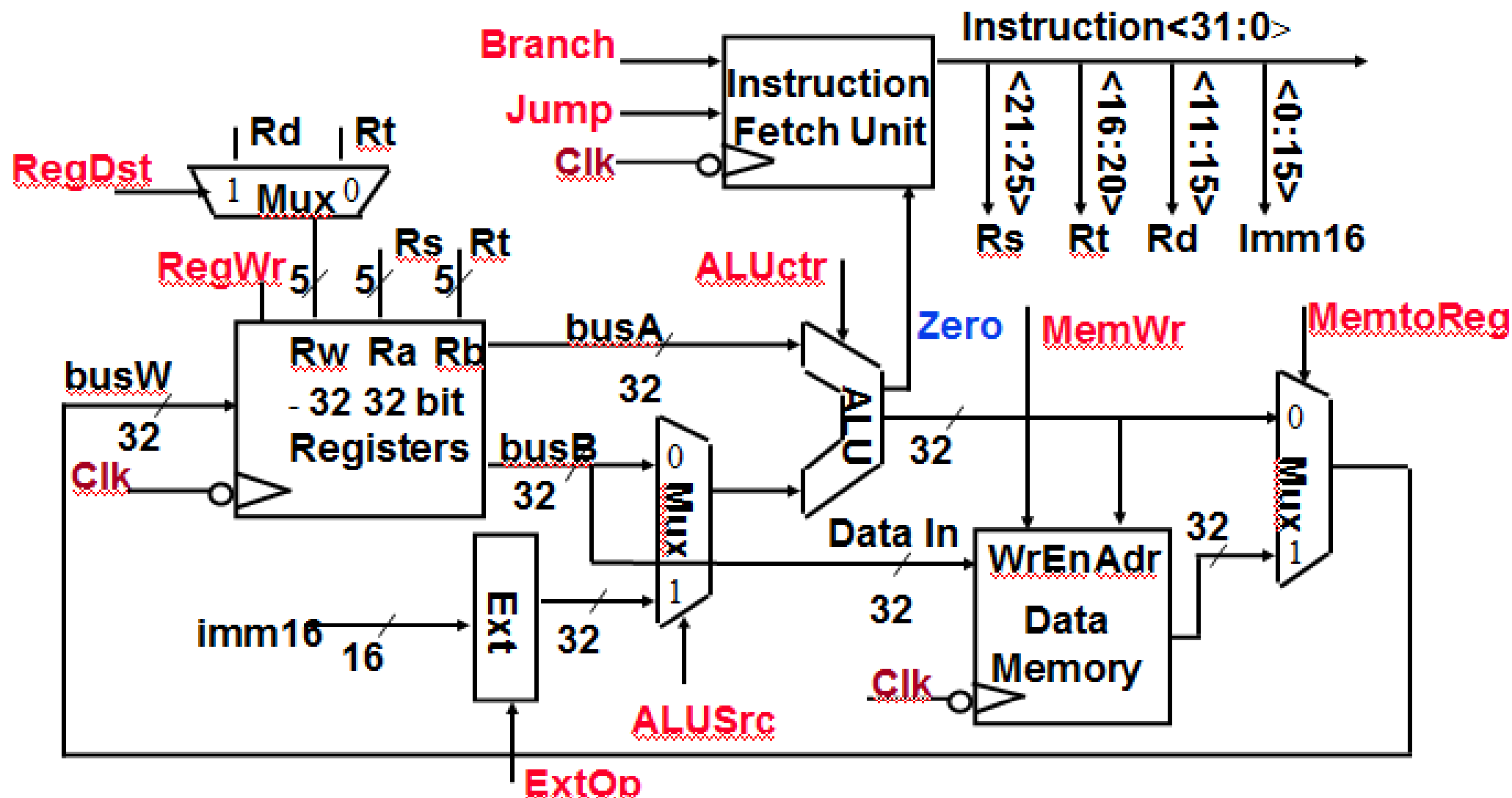- 假定图中单周期数据通路对应的控制逻辑发生错误，使得在任何情况下控制信号RegWr、RegDst、Branch、MemWr、ExtOp 总是为0，则哪些指令不能正确执行？为什么？



下一节

- 微程序控制器 vs 硬连线控制器
- 请预习到 5.5

再见

